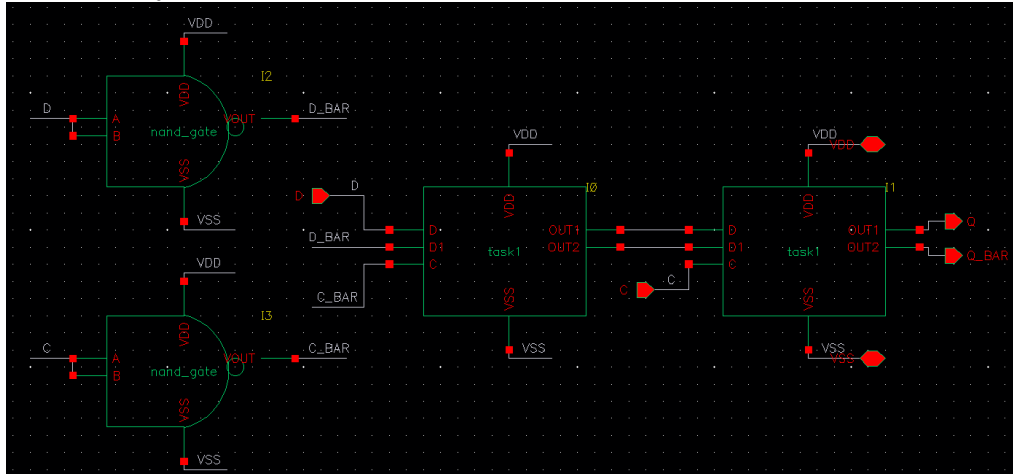



Analog Flow:

Apart from spice simulation and characterization of CMOS circuits, I also designed the schematic and layout of a D-type flip flop using Cadence Virtuoso as shown below.


- Internals of the symbol:




- Test Circuit:

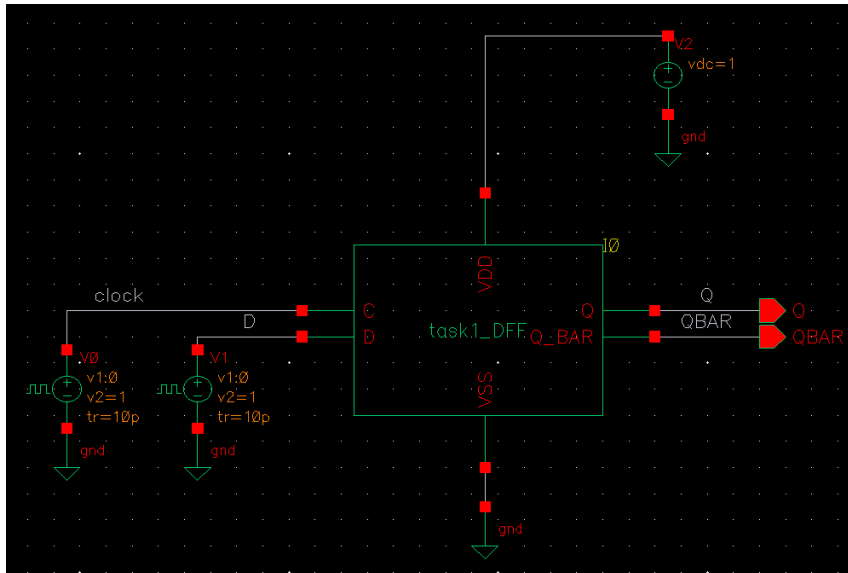


- Plot:

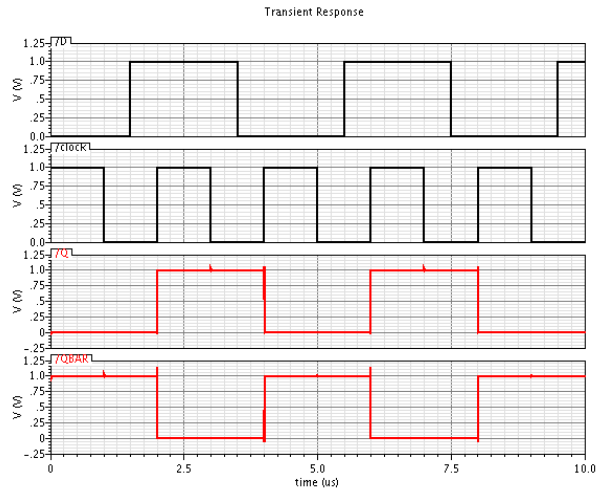


- Layout:

 


- DRC Results:

 


- LVS Results:

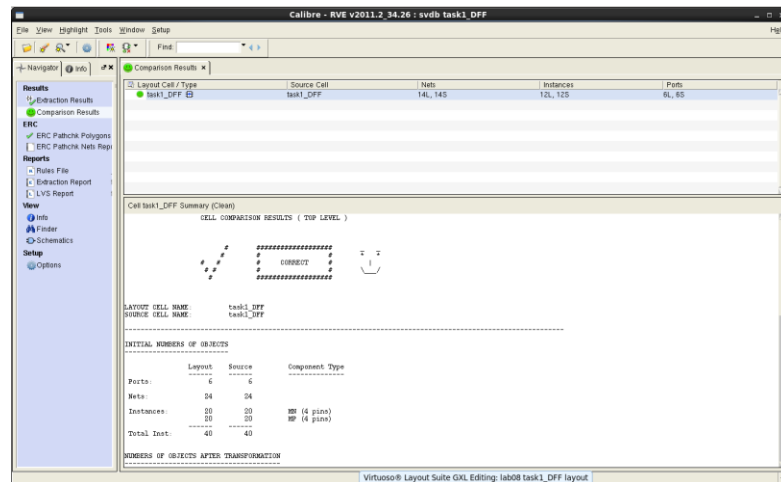

- Layout of an Individual latch:

 

- Layout of an individual NAND Gate:

 

Digital Flow:

Physical layout of a 16*1 mux using the netlist synthesized from the Verilog code.

- Netlist

```

// (data 2[0]), .C (n_5), .Z (n_24));
A0221D0 g862(.A1 (n_33), .A2 (data_0[0]), .B1 (n_32), .B2
(data 2[0]), .C (n_3), .Z (n_23));
A0221D0 g867(.A1 (n_33), .A2 (data_0[1]), .B1 (n_32), .B2
(data 2[1]), .C (n_4), .Z (n_22));
A0221D0 g859(.A1 (n_33), .A2 (data_0[13]), .B1 (n_32), .B2
(data 2[13]), .C (n_12), .Z (n_21));
A0221D0 g860(.A1 (n_33), .A2 (data_0[4]), .B1 (n_32), .B2
(data 2[4]), .C (n_10), .Z (n_20));
A0221D0 g863(.A1 (n_33), .A2 (data_0[2]), .B1 (n_32), .B2
(data 2[2]), .C (n_6), .Z (n_19));
A0221D0 g859(.A1 (n_33), .A2 (data_0[11]), .B1 (n_32), .B2
(data 2[11]), .C (n_1), .Z (n_18));
A022D0 q875(.A1 (n_15), .A2 (data_1[10]), .B1 (data_3[10]), .B2
(n_14), .Z (n_17));
A022D0 q886(.A1 (n_15), .A2 (data_1[6]), .B1 (data_3[6]), .B2 (n_14),
.Z (n_16));
A022D0 q873(.A1 (n_15), .A2 (data_1[3]), .B1 (data_3[3]), .B2 (n_14),
.Z (n_13));
A022D0 q874(.A1 (n_15), .A2 (data_1[13]), .B1 (data_3[13]), .B2
(n_14), .Z (n_12));
A022D0 q807(.A1 (n_15), .A2 (data_1[11]), .B1 (data_3[11]), .B2
(n_14), .Z (n_11));
A022D0 q876(.A1 (n_15), .A2 (data_1[4]), .B1 (data_3[4]), .B2 (n_14),
.Z (n_10));
A022D0 q877(.A1 (n_15), .A2 (data_1[5]), .B1 (data_3[5]), .B2 (n_14),
.Z (n_9));
A022D0 q878(.A1 (n_15), .A2 (data_1[15]), .B1 (data_3[15]), .B2
(n_14), .Z (n_8));
A022D0 q803(.A1 (n_15), .A2 (data_1[12]), .B1 (data_3[12]), .B2
(n_14), .Z (n_7));
A022D0 q880(.A1 (n_15), .A2 (data_1[2]), .B1 (data_3[2]), .B2 (n_14),
.Z (n_6));
A022D0 q881(.A1 (n_15), .A2 (data_1[8]), .B1 (data_3[8]), .B2 (n_14),
.Z (n_5));
A022D0 q882(.A1 (n_15), .A2 (data_1[14]), .B1 (data_3[14]), .B2
(n_14), .Z (n_4));
A022D0 q879(.A1 (n_15), .A2 (data_1[9]), .B1 (data_3[9]), .B2 (n_14),
.Z (n_3));
A022D0 q804(.A1 (n_15), .A2 (data_1[0]), .B1 (data_3[0]), .B2 (n_14),
.Z (n_2));
A022D0 q805(.A1 (n_15), .A2 (data_1[1]), .B1 (data_3[1]), .B2 (n_14),
.Z (n_1));
A022D0 q886(.A1 (n_15), .A2 (data_1[7]), .B1 (data_3[7]), .B2 (n_14),
.Z (n_0));
INR2D0 q809(.A1 (select[1]), .B1 (select[0]), .ZN (n_32));
NR2D0 q890(.A1 (select[1]), .A2 (select[0]), .ZN (n_33));
INR2D0 q891(.A1 (select[0]), .B1 (select[0]), .ZN (n_15));
CRAN2D1 g892(.A1 (select[1]), .A2 (select[0]), .Z (n_14));
BUFF016 drc_bufs(.T (n_47), .Z (mux_out[15]));
endmodule

```

```

// Generated by Cadence Genus(TM) Synthesis Solution 19.14-s110.1
// Generated on: May 26 2022 21:49:18 PKT (May 26 2022 16:49:18 UTC)

// Verification Directory fw/Mux_16_bit

module Mux_16_bit(mux_out, data_3, data_2, data_1, data_0, enable,
    select);
    input [15:0] data_3, data_2, data_1, data_0;
    input enable;
    input [1:0] select;
    output [15:0] mux_out;
    wire [15:0] data_3, data_2, data_1, data_0;
    wire enable;
    wire [1:0] select;
    wire [15:0] mux_out;
    wire n_0, n_1, n_2, n_3, n_4, n_5, n_6, n_7;
    wire n_8, n_9, n_10, n_11, n_12, n_13, n_14, n_15;
    wire n_16, n_17, n_18, n_19, n_20, n_21, n_22, n_23;
    wire n_24, n_25, n_26, n_27, n_28, n_29, n_30, n_31;
    wire n_32, n_33, n_34, n_35, n_47;
    BUFTD16 g16(.I (n_29), .OE (enable), .Z (mux_out[12]));
    BUFTD16 g16(.I (n_22), .OE (enable), .Z (mux_out[13]));
    BUFTD16 g30(.I (n_23), .OE (enable), .Z (mux_out[14]));
    BUFTD16 g17(.I (n_21), .OE (enable), .Z (mux_out[15]));
    AND2D1 g95(.A1 (n_34), .A2 (enable), .Z (n_47));
    BUFTD16 g19(.I (n_31), .OE (enable), .Z (mux_out[1]));
    BUFTD16 g20(.I (n_28), .OE (enable), .Z (mux_out[10]));
    BUFTD16 g21(.I (n_23), .OE (enable), .Z (mux_out[9]));
    BUFTD16 g26(.I (n_28), .OE (enable), .Z (mux_out[4]));
    BUFTD16 g23(.I (n_27), .OE (enable), .Z (mux_out[7]));
    BUFTD16 g24(.I (n_30), .OE (enable), .Z (mux_out[8]));
    BUFTD16 g25(.I (n_26), .OE (enable), .Z (mux_out[5]));
    BUFTD16 g22(.I (n_24), .OE (enable), .Z (mux_out[11]));
    BUFTD16 g27(.I (n_35), .OE (enable), .Z (mux_out[3]));
    BUFTD16 g28(.I (n_19), .OE (enable), .Z (mux_out[2]));
    BUFTD16 g29(.I (n_18), .OE (enable), .Z (mux_out[14]));
    A0221D0 g857(.A1 (n_33), .A2 (data_0[1]), .B1 (n_32), .B2
    (data_2[1]), .C (n_13), .Z (n_35));
    A0221D0 g870(.A1 (n_33), .A2 (data_0[15]), .B1 (n_32), .B2
    (data_2[15]), .C (n_8), .Z (n_34));
    A0221D0 g871(.A1 (n_33), .A2 (data_0[11]), .B1 (n_32), .B2
    (data_2[11]), .C (n_11), .Z (n_31));
    A0221D0 g872(.A1 (n_33), .A2 (data_0[6]), .B1 (n_32), .B2
    (data_2[6]), .C (n_16), .Z (n_30));
    A0221D0 g864(.A1 (n_33), .A2 (data_0[11]), .B1 (n_32), .B2
    (data_2[12]), .C (n_7), .Z (n_29));
    A0221D0 g858(.A1 (n_33), .A2 (data_0[10]), .B1 (n_32), .B2
    (data_2[10]), .C (n_17), .Z (n_28));
    A0221D0 g865(.A1 (n_33), .A2 (data_0[7]), .B1 (n_32), .B2
    (data_2[7]), .C (n_0), .Z (n_27));
    A0221D0 g861(.A1 (n_33), .A2 (data_0[5]), .B1 (n_32), .B2
```

- Layout

