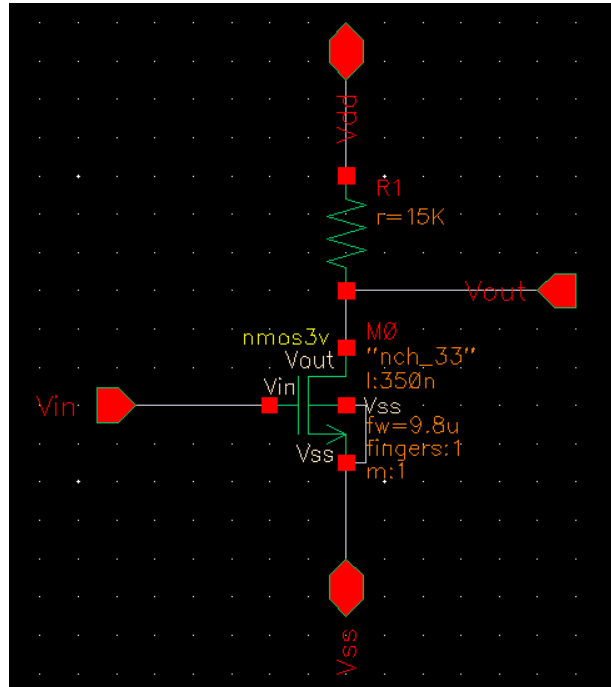



## Lab Task:

**Task#1:** Transient analysis of CS amplifier.


Internals of the symbol:



Testbench circuit:

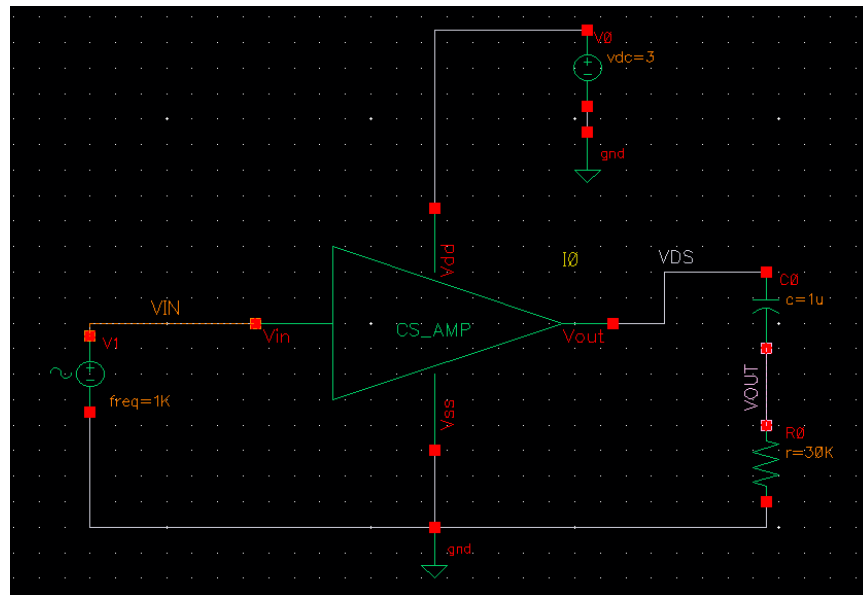


Input Vs Output:

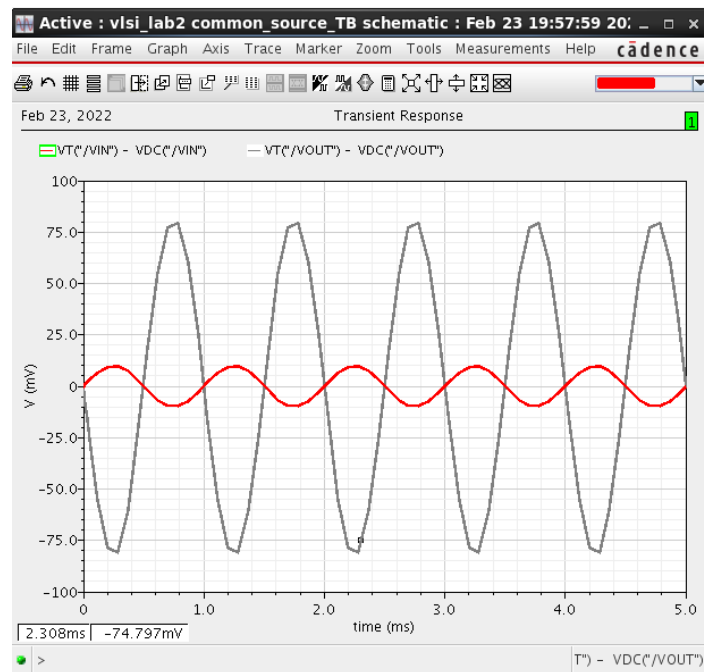


**Task#2:** Ac analysis of CS amplifier.


Internals of the symbol:

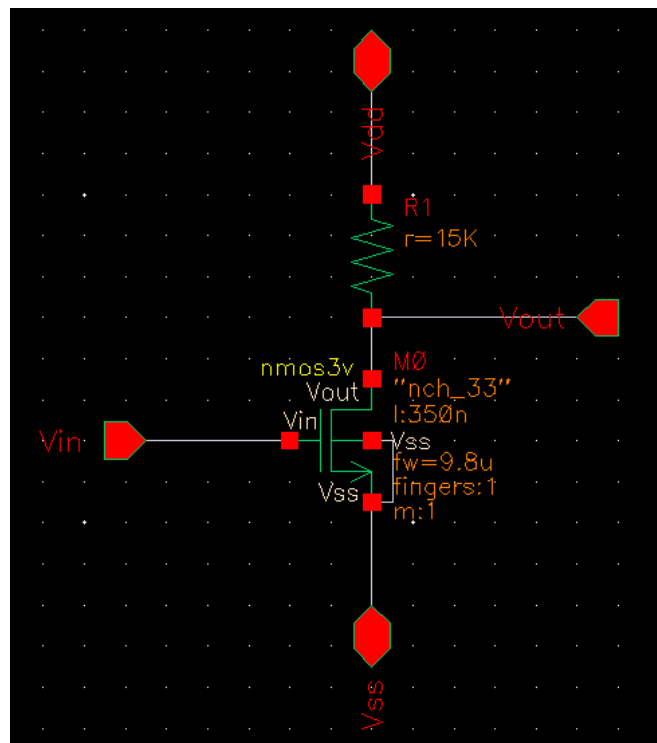

Testbench circuit:

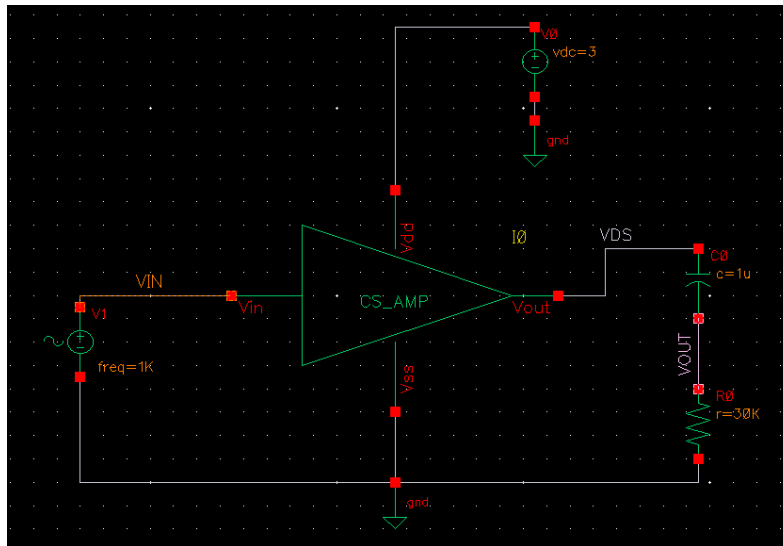

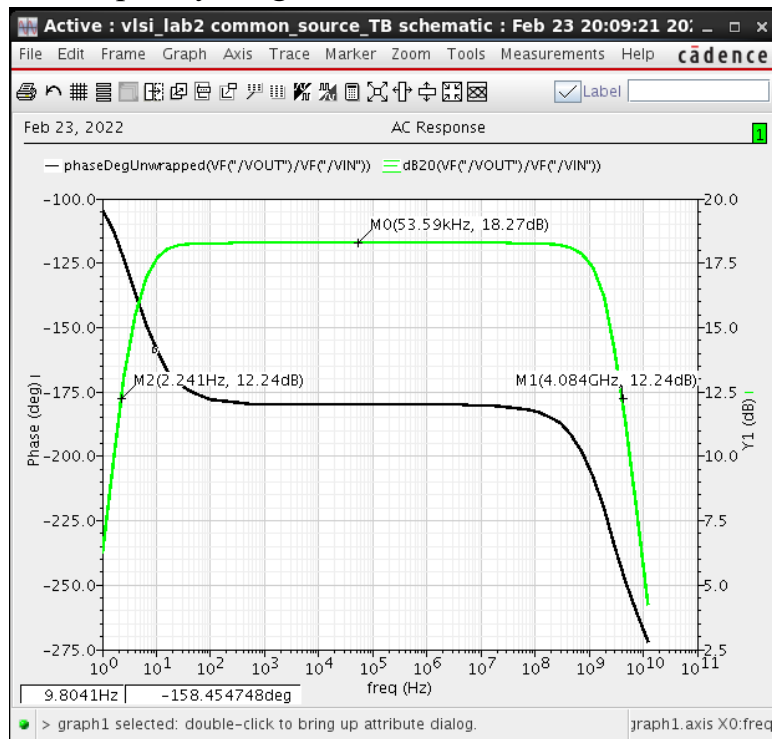
Gain and phase for a frequency range of 1Hz - 12 GHz:




## Lab Assignments:

**Task#1:** Transient & Ac analysis of CG amplifier.


Internals of the symbol:

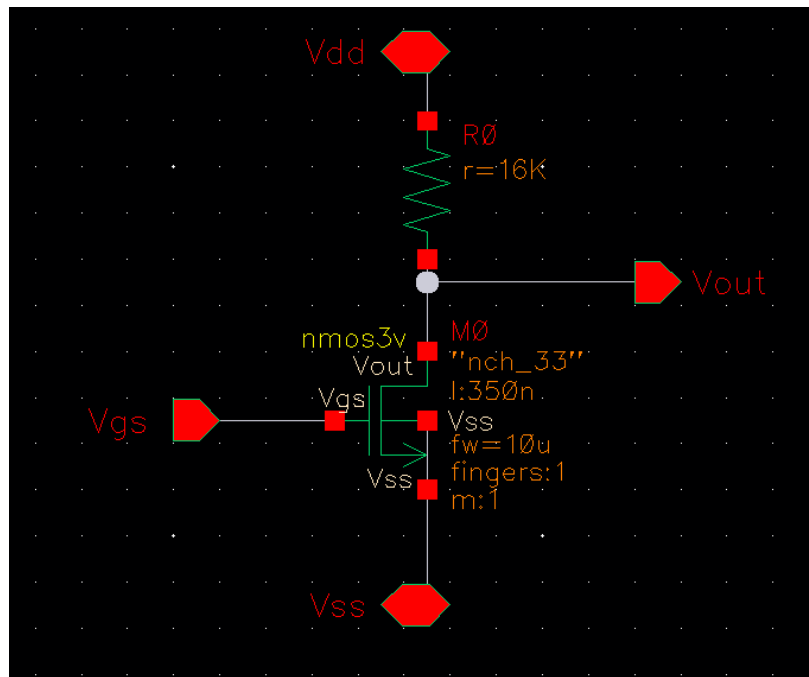


Testbench circuit:

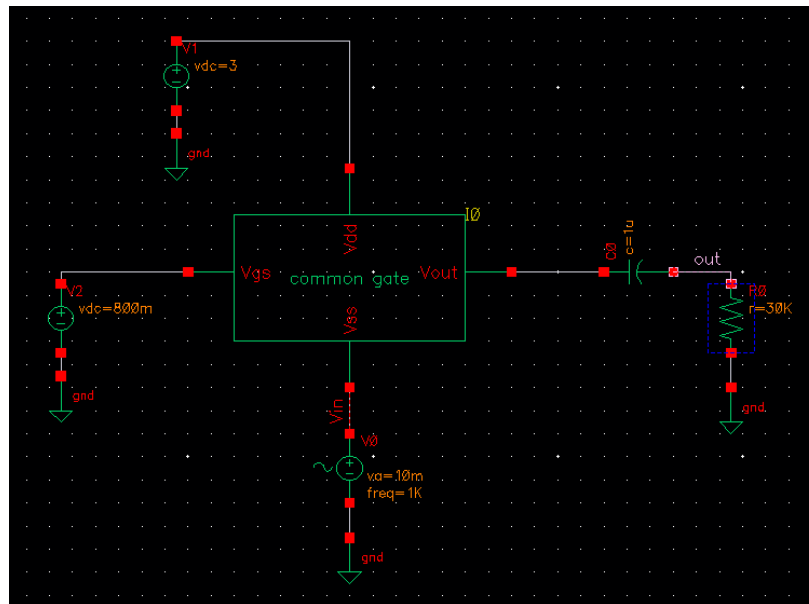

Input Vs Output:

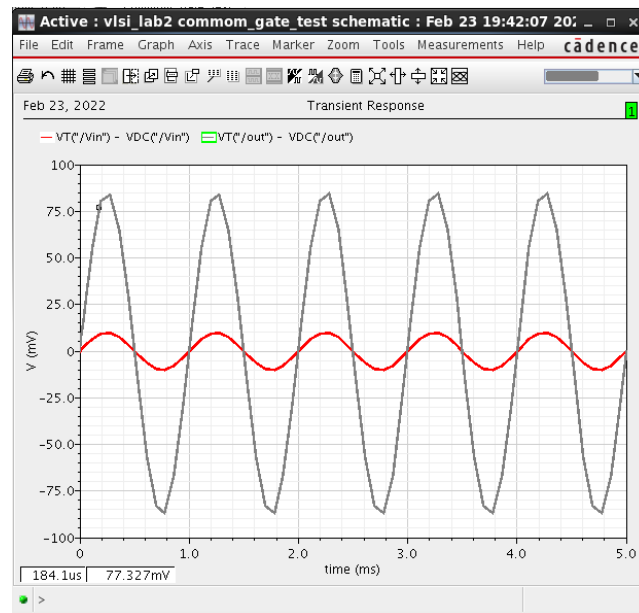


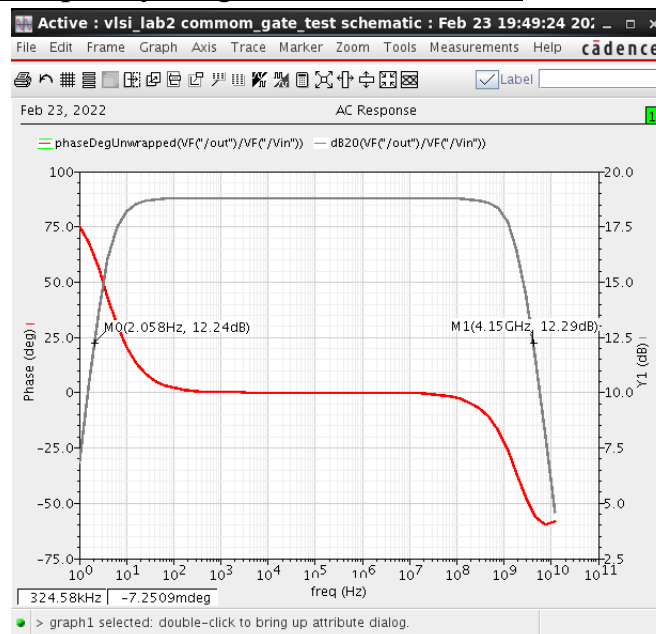Gain and phase for a frequency range of 1Hz - 12 GHz:




**Task#2:** Effect of different load capacitance on CS amplifier.


1) 100 nF

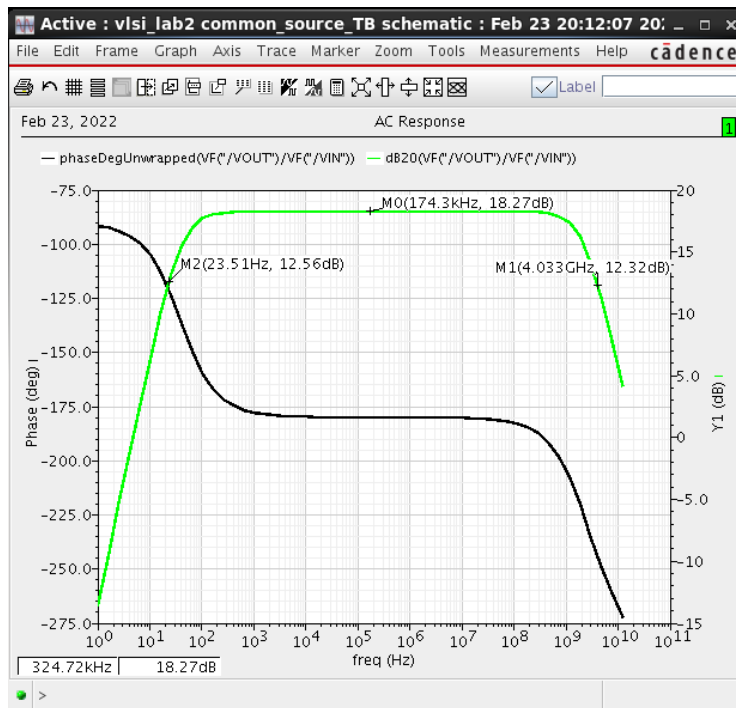

2) 1  $\mu$ F

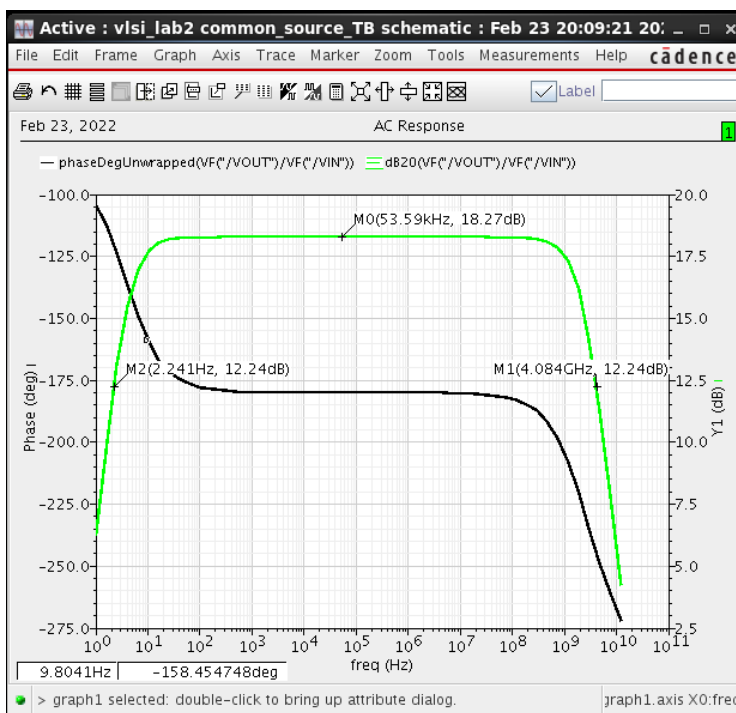

3) 10  $\mu$ F

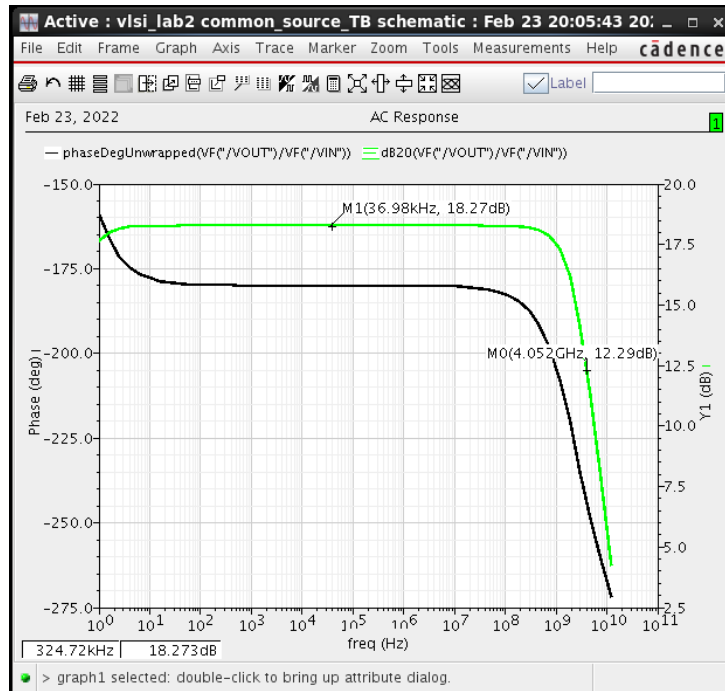

**Observation:** It is observed that the mid-band gain remained the same in all three cases but the bandwidth increased with effective movement in the lower cutoff frequency towards 0 Hz as we increased the capacitance.